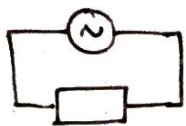


AC Circuits



example: simple resistor circuit



The AC generator provides $V = V_0 \sin \omega t$
so the current is given by:


$$I = \frac{V}{R} = \frac{V_0}{R} \sin \omega t$$

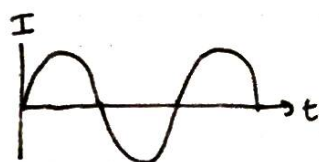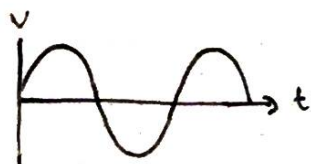since both I and V are sine waves, they are in phase:



The two waves are in phase with each other

example: simple inductor circuit

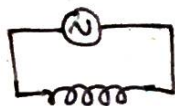

The AC generator provides $V = V_0 \sin \omega t$
so the current is given by:

$$L \frac{dI}{dt} = V \Rightarrow \frac{dI}{dt} = \frac{V_0 \sin \omega t}{L}$$


$$\int dI = \int \frac{V_0}{L} \sin \omega t \, dt$$

$$I = -\frac{V_0}{\omega L} \cos \omega t + \text{constant}$$

$$I = \frac{V_0}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

↑ phase shift

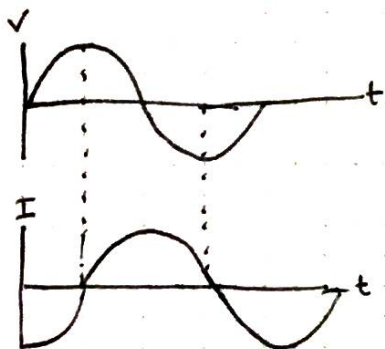← This is the DC offset which is 0 in this case



The two waves are out of phase with each other by $\frac{\pi}{2}$

The current lags behind the voltage

example: simple capacitor circuit




The AC generator provides $V = V_0 \sin \omega t$
so the current is given by:

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt} \Rightarrow I = C \frac{d}{dt} V_0 \sin \omega t$$


$$I = CV_0 \omega \cos \omega t = CV_0 \omega \sin(\omega t + \frac{\pi}{2})$$

↑ phase shift

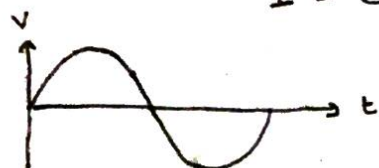

The two are out of phase by $\frac{\pi}{2}$

The current leads the voltage

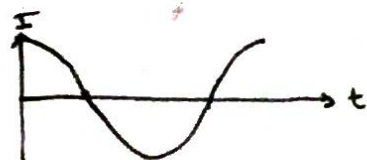


A good way to remember these for inductor and capacitor circuits is by the mnemonic CIVIL

for C: IV (current leads voltage)

for L: VI (voltage leads current)

example: LC circuit

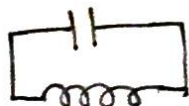

Using Kirchoff's voltage Law:

$$L \frac{dI}{dt} + \frac{q}{C} = 0 \Rightarrow L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0$$

$$\therefore \frac{d^2 q}{dt^2} = -\frac{1}{LC} q$$


This is an equation for simple harmonic motion: $\frac{d^2 q}{dt^2}$ is like acceleration here.

The solution is: $q = q_0 \cos(\omega t + \delta)$

with $\omega^2 = \frac{1}{LC}$

The charge leaves the capacitor but the inductor reloads it onto the capacitor.

example: LCR discharge circuit

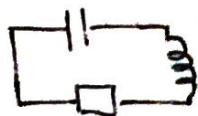


using Kirchhoff's Voltage Law:

$$L \frac{dI}{dt} + \frac{q}{C} + IR = 0$$


$$\Rightarrow L \frac{d^2q}{dt^2} + \frac{q}{C} + R \frac{dq}{dt} = 0$$

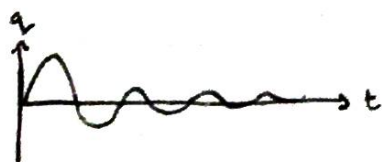This has solution $q = q_0 e^{-Rt/2L} \cos \omega t$
and is equivalent to damped harmonic motion:



The resistor damps the SHM by removing energy from the circuit as heat.

example: Driver LCR circuit

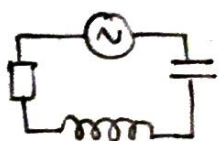

The AC generator provides a current of $I = I_0 \cos \omega t$ so the voltage drops in each component are:

$$V_R = I_0 R \cos \omega t$$

$$V_L = I_0 L \omega \cos(\omega t + \frac{\pi}{2}) = I_0 L \omega \sin \omega t$$

$$V_C = \frac{I_0}{\omega C} \cos(\omega t - \frac{\pi}{2}) = -\frac{I_0}{\omega C} \sin \omega t$$

This can be found using CIVIL or by using calculus.


$$V_S = V_R + V_L + V_C \Rightarrow V_S = I_0 R \cos \omega t + I_0 \left(L\omega - \frac{1}{\omega C} \right) \sin \omega t$$

Write this in the form:


$$\sqrt{A^2 + B^2} \left[\frac{A}{\sqrt{A^2 + B^2}} \cos \omega t + \frac{B}{\sqrt{A^2 + B^2}} \sin \omega t \right]$$

where $A = I_0 R$ and $B = I_0 \left(L\omega - \frac{1}{\omega C} \right)$

Now we can draw the triangle:

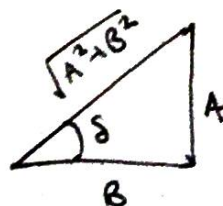

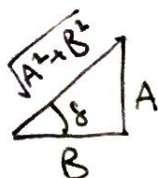The reason for drawing the triangle is to obtain expressions for the terms in the voltage equation.



$$\frac{A}{\sqrt{A^2 + B^2}} = \frac{\text{opposite}}{\text{hypotenuse}} = \sin \delta$$

$$\frac{B}{\sqrt{A^2 + B^2}} = \frac{\text{adjacent}}{\text{hypotenuse}} = \cos \delta$$

$$\therefore V_s = \sqrt{A^2 + B^2} \left[\frac{A}{\sqrt{A^2 + B^2}} \cos \omega t + \frac{B}{\sqrt{A^2 + B^2}} \sin \omega t \right]$$

$$V_s = \sqrt{A^2 + B^2} [\sin \delta \cos \omega t + \cos \delta \sin \omega t]$$

$$\therefore \underline{V_s = \sqrt{A^2 + B^2} \sin(\omega t + \delta)}$$


Since this is in the form $V_s = V_0 \sin \omega t$

$$V_0 = \sqrt{A^2 + B^2}$$

$$V_0^2 = (I_0 R)^2 + I_0^2 \left(\omega L - \frac{1}{\omega C} \right)^2$$

$$\Rightarrow I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$

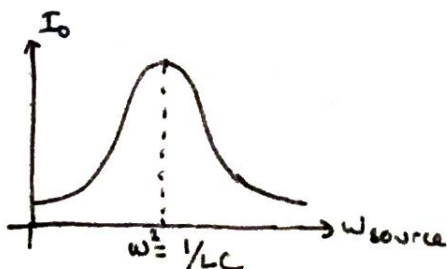This shows that there is a peak I_0 , a "resonance", when the driving frequency matches the SHM frequency of the LC circuit.



The peak is seen here when $\omega^2 = \frac{1}{LC}$ as for the SHM circuit.